




KINGDOM OF SAUDI ARABIA | JAZAN UNIVERSITY
COLLEGE OF COMPUTER SCIENCE & INFORMATION TECHNOLOGY

LAB Exam 2022-2023, Second Semester

Academic Year	2022 -2023	Total Marks	20
Course with code	ITEC-252- Digital Design & Computer Architecture, LEVEL-4	Section	2051
Date of EXAM	7-2-2023	Duration	24 hrs.
STUDENT NAME:		STUDENT ID:	

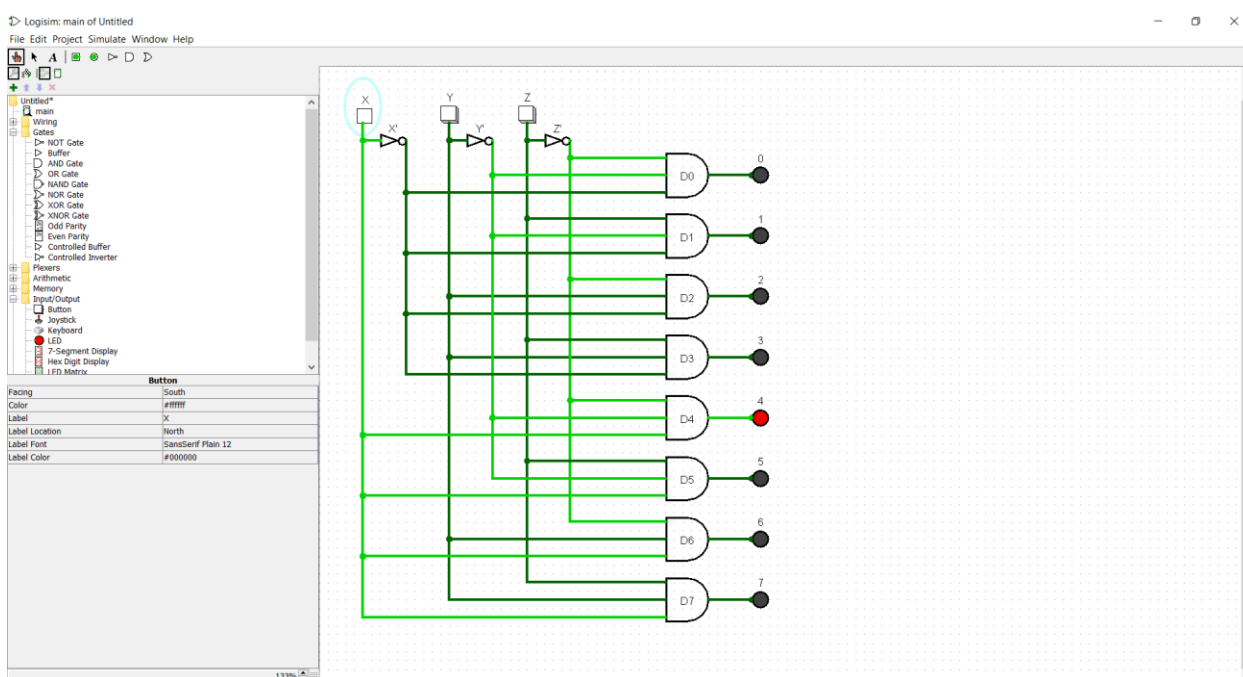1. Use Logisim to draw the circuit diagram and write the truth table of the 3-to-8 Line Decoder using AND gate.



Here's the truth table for a 3-to-8 line decoder:



Input X	Input Y	Input Z	Output D0	Output D1	Output D2	Output D3	Output D4	Output D5	Output D6	Output D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0

0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


2. Use Logisim to simulate the figure below and write the expression for the Boolean Function. Verify the circuit operation and fill in its truth table.



$(\neg A \& B) \text{ xor } (A \mid C)$

A	B	C	$(\neg A \& B)$	$(A \mid C)$	Output
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	0	1	1
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	0	1	1

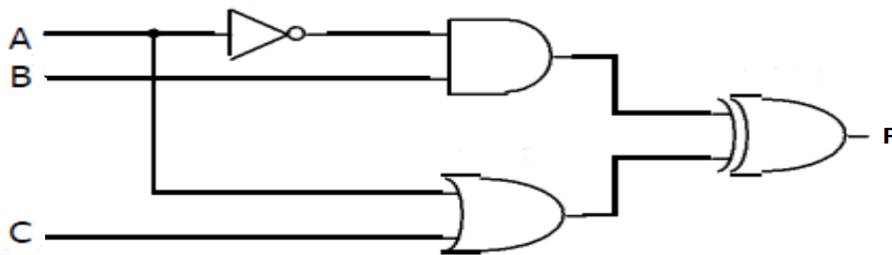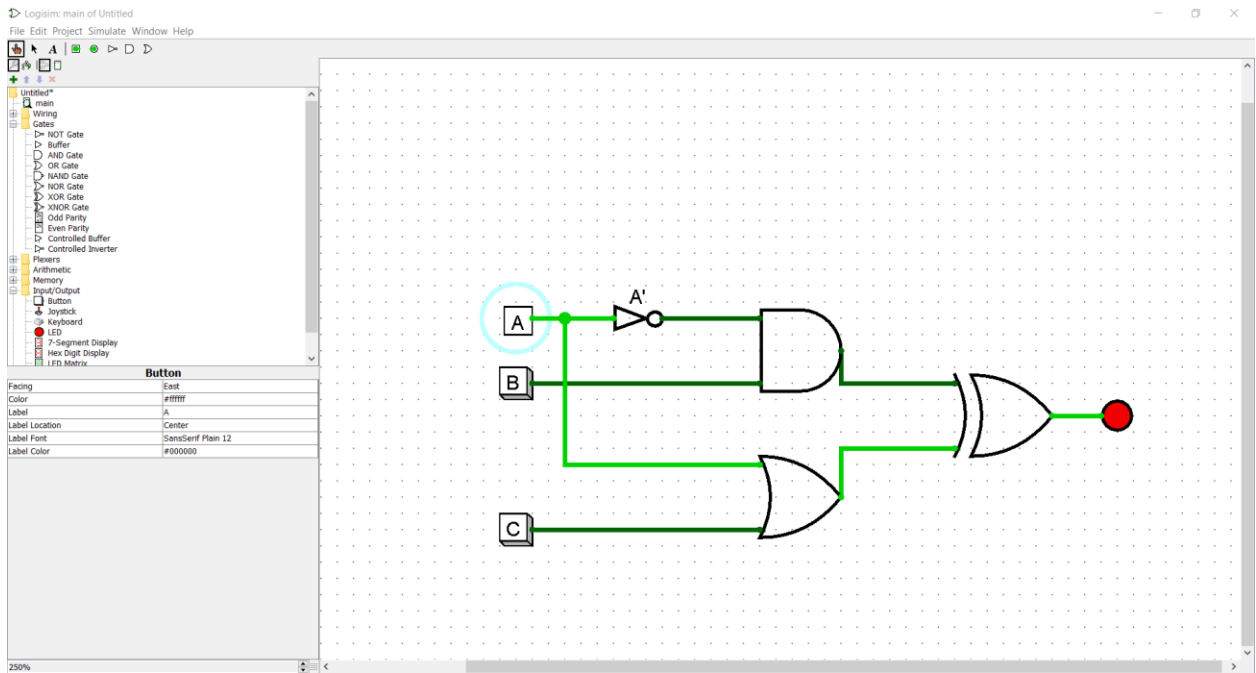


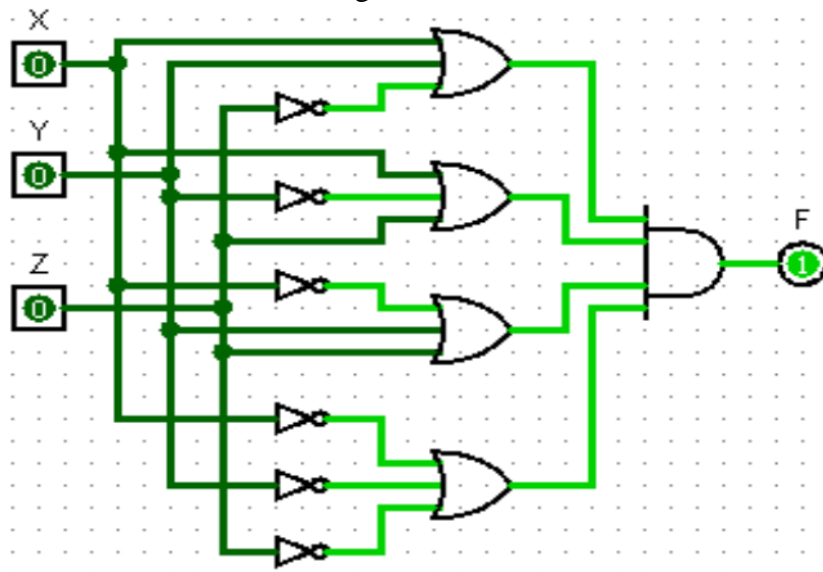
3. Use Logisim software to simulate the figure below.



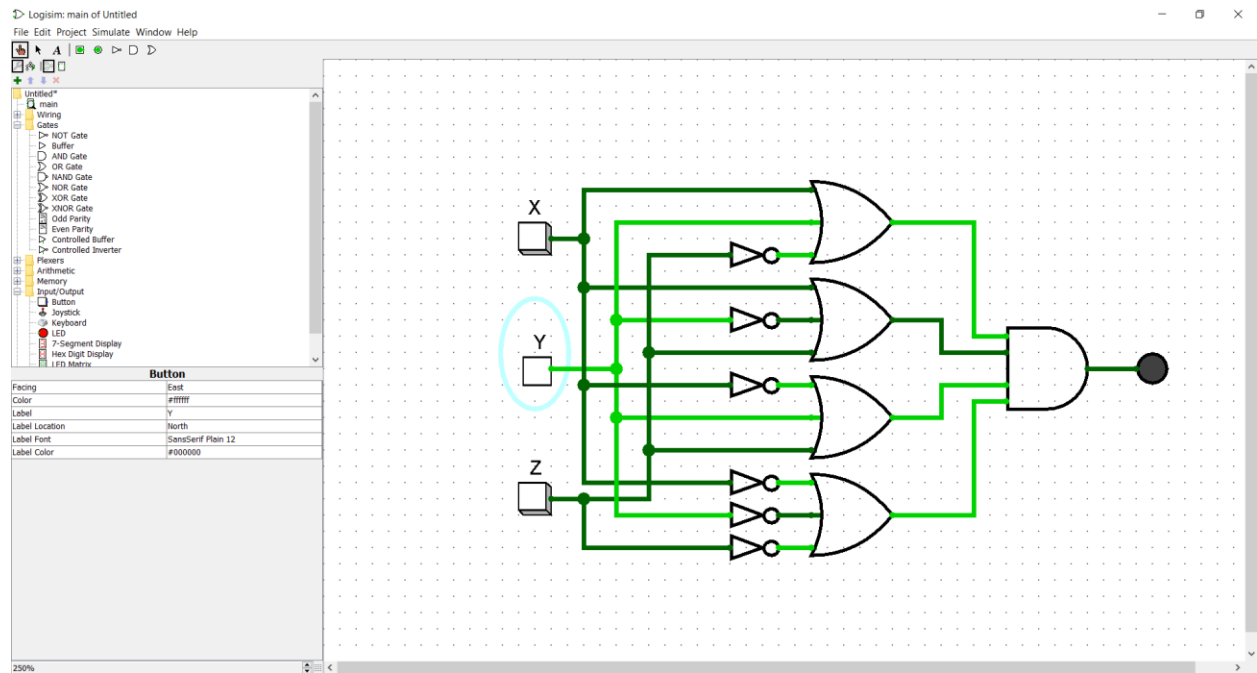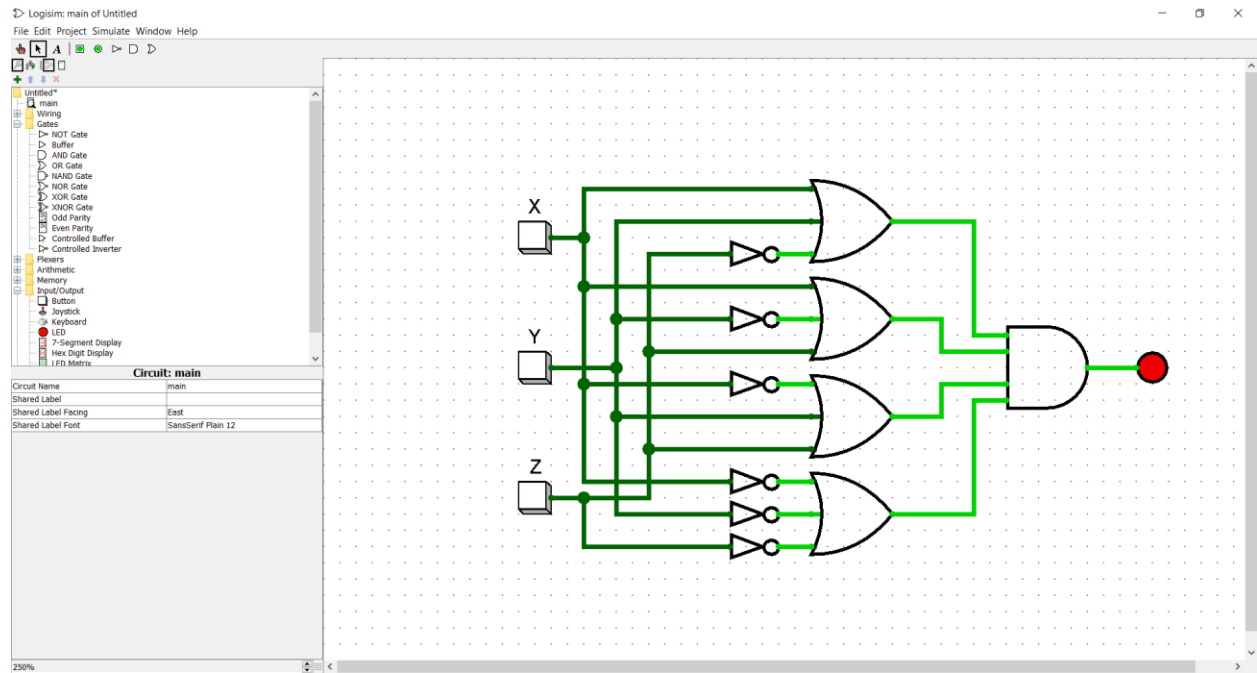


4. Using Logisim software to draw circuit diagram for the following equation:

$$K = m'w + mw'$$

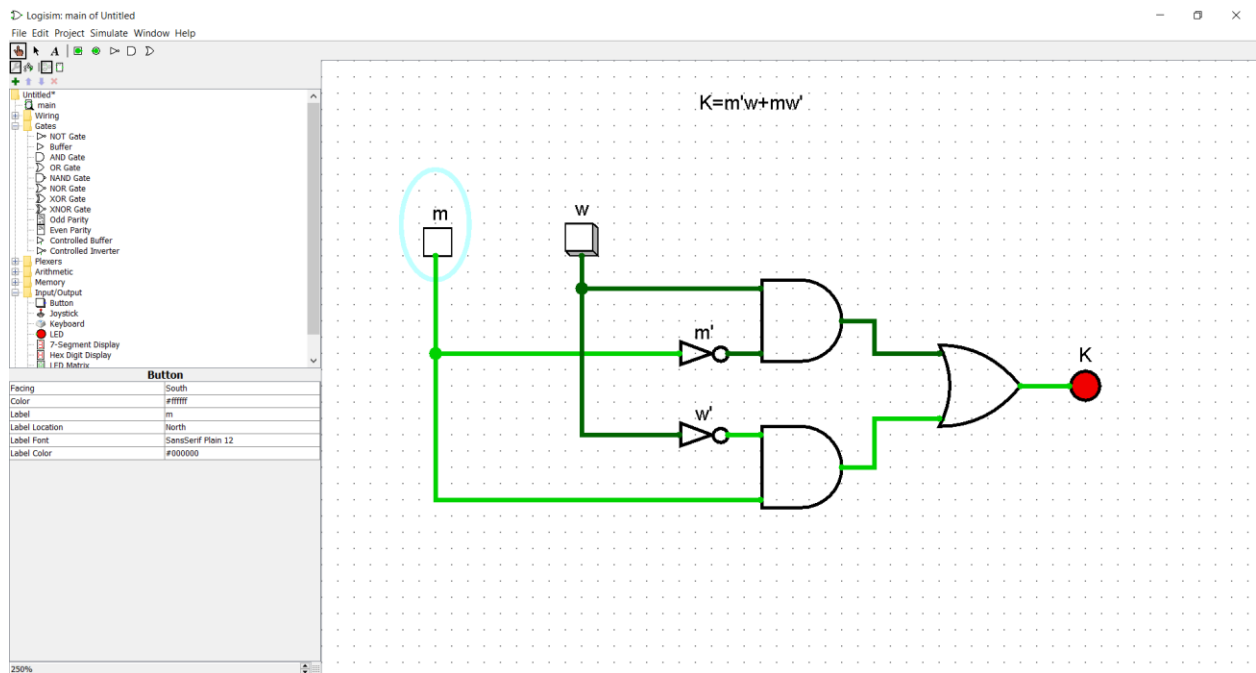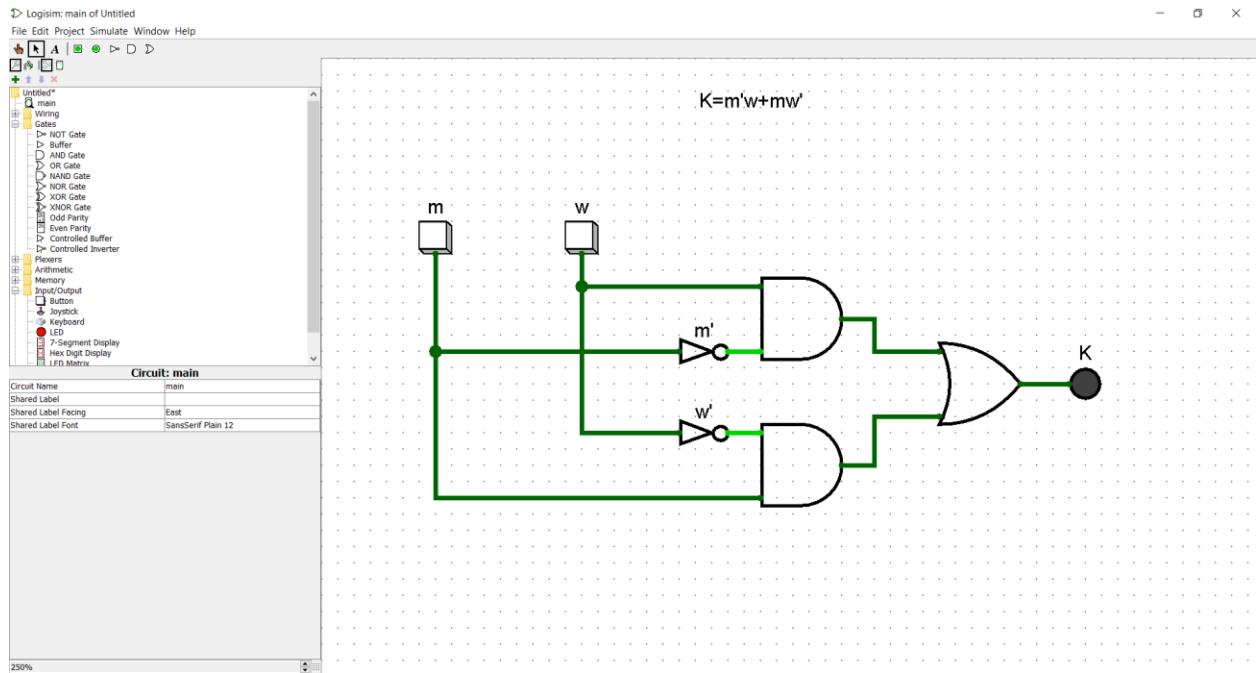



5. Using Logisim software to draw circuit diagram for the following equation:

$$Y = (A + B)(B + C)(A + C')$$

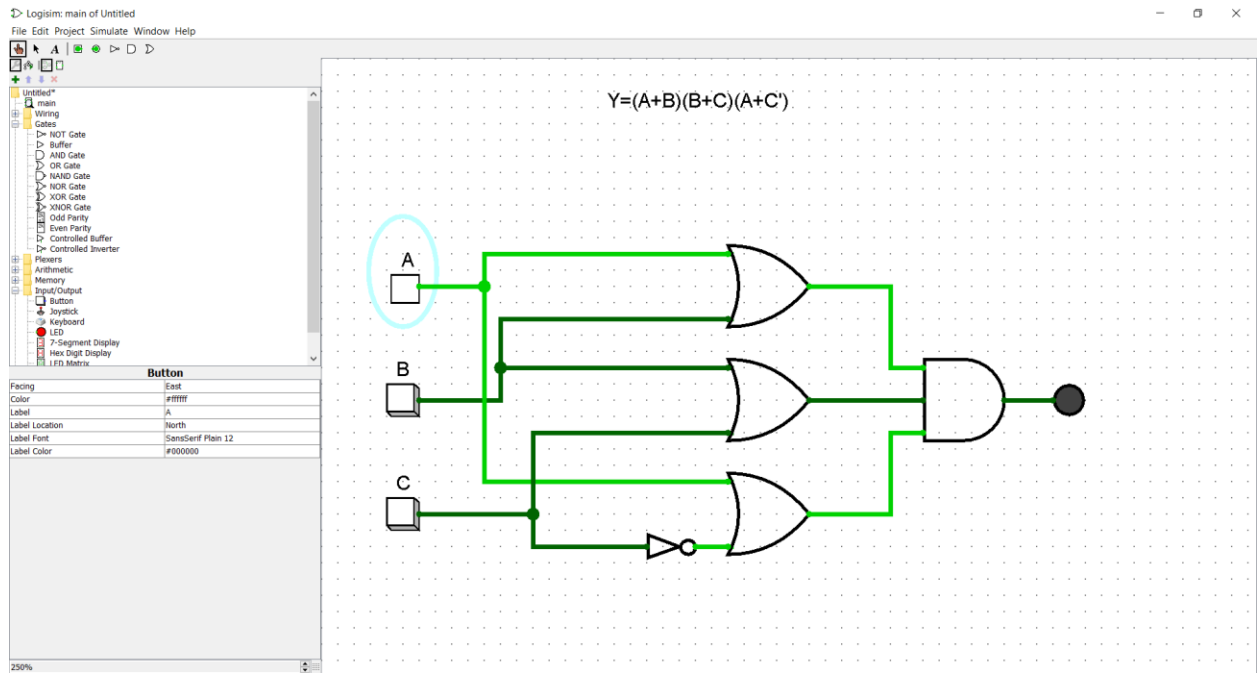

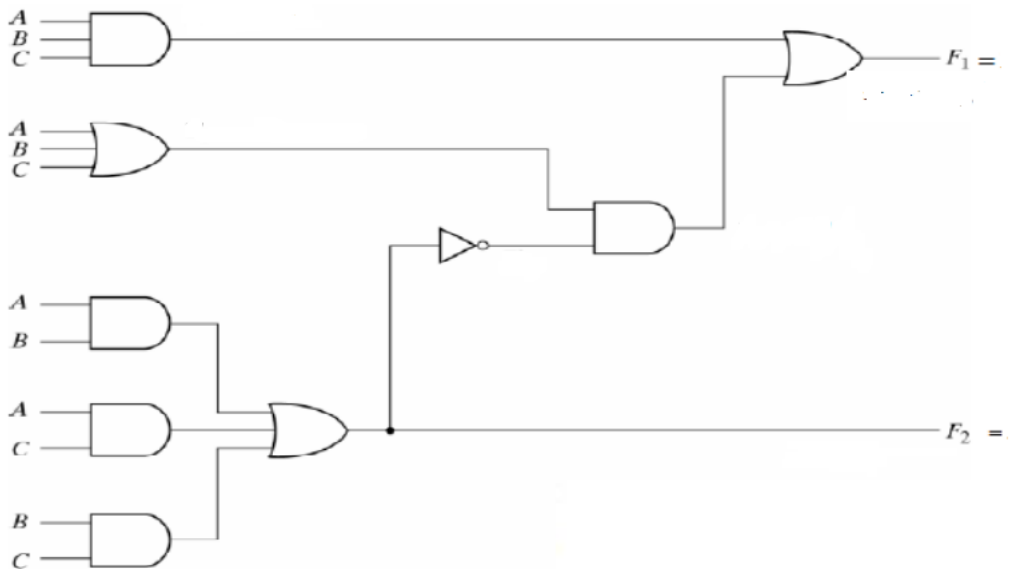6. Use Logisim software to simulate the figure below and write the expression for the Boolean Function for both F_1 and F_2 .



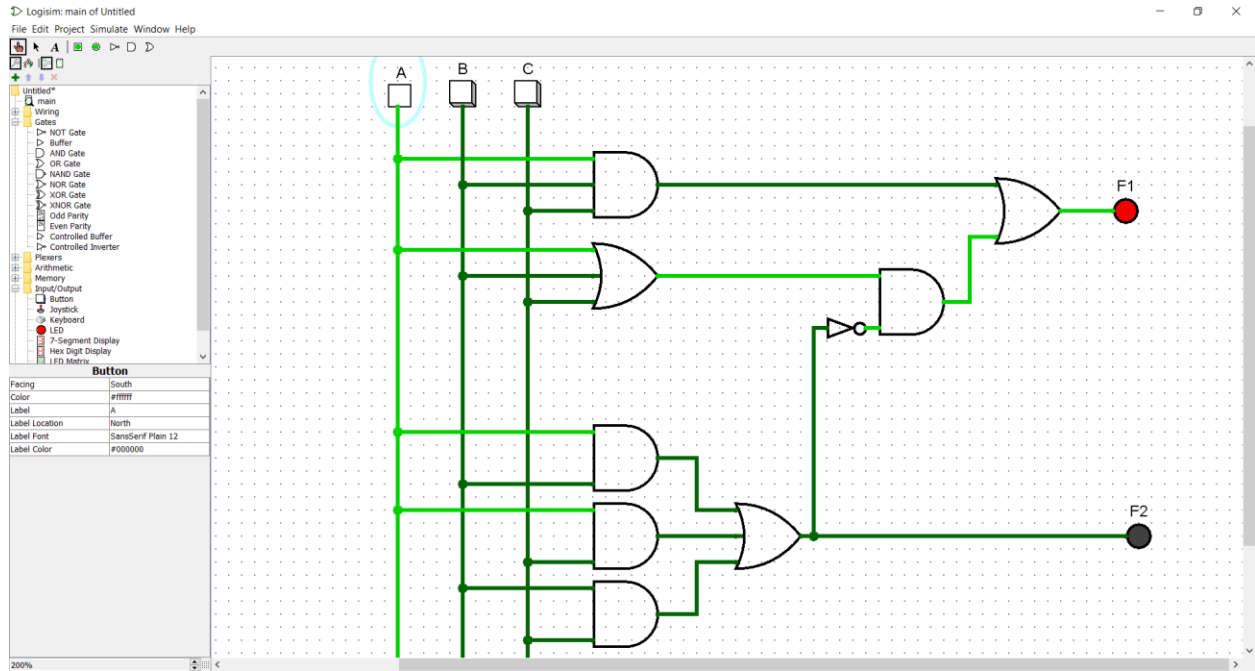

Goodluck

Instructions:

- Upload the implementation file from Logisim for each question (*by the name of the question*).
- The screenshots of all the simulations must be included.
- Complete the tasks and submit the task (implementation files) on Blackboard in time.
- Include snapshots from your simulations in your answer sheet for each question.
- Do not submit via email or WhatsApp.
- Cheating will be detected by Plagiarism software and will cause a deduction in marks.